

## BIAS COMPENSATION

In bias stabilization circuits, the negative feedback improves the stability of the operating point but at the same time it reduces the gain of the amplifier. In certain applications, the loss in the gain becomes serious drawback and is intolerable.

In such cases, compensation techniques are used to reduce the drift of the operating point. Sometimes for excellent bias and thermal stabilization both stabilization as well as compensation techniques are used.


Stabilization techniques refer to the use of resistive biasing whereas compensation techniques refer to the use of temperature sensitive devices such as diodes, transistors, thermistors etc. to compensate for variations in current.

(1) Diode compensation for instability due to  $V_{BE}$  variation:


Used for silicon transistors, where the changes of  $V_{BE}$  with temp make changes significantly in  $I_C$ .

A diode may be used as compensation element.

(2)

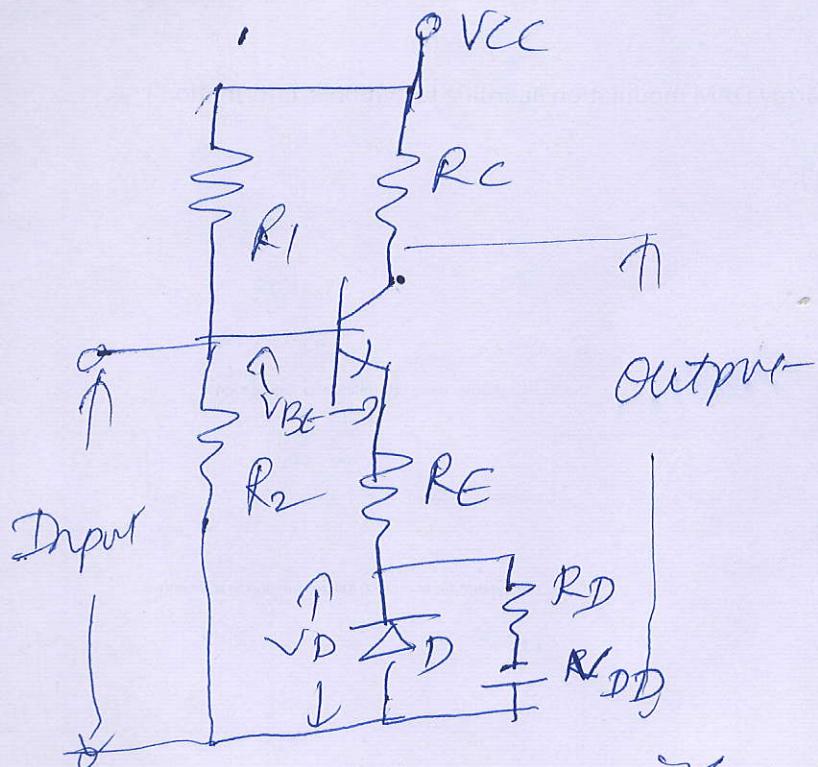

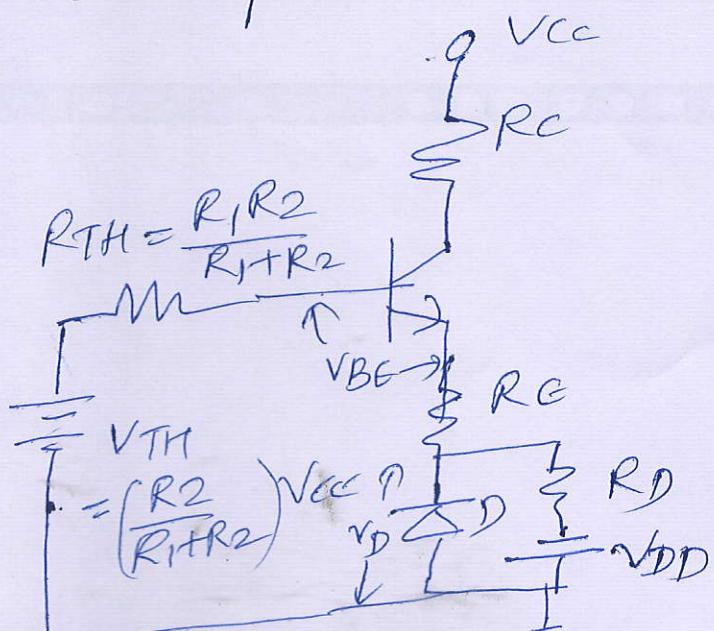(a) Voltage divider bias with stabilization and compensation



(b) Thevenin's equivalent circuit  
 The diode D used here is of the same material and type as the transistor. Hence the voltage  $V_D$  across the diode has same temperature coefficient as  $V_{BE}$  of the transistor. The diode is forward biased by the source  $V_{DD}$  and resistor  $R_D$ .

So when  $V_{BE}$  changes by  $\Delta V_{BE}$  with change in temperature  $V_D$  changes by  $\Delta V_D$ . The change tend to cancel each other.

- Applying KVL to base circuit.

$$V_{TH} - V_{BE} + V_D = I_B R_{TH} + R_E (I_B + I_C) \quad \dots (1)$$

$$\text{But } I_C = \beta I_B + (1 + \beta) I_{CO} \quad \dots (2)$$

$$\therefore I_B = \frac{I_C - (1 + \beta) I_{CO}}{\beta}$$

$$V_{TH} - V_{BE} + V_D = R_E I_C + (R_{TH} + R_E) I_B$$

Substitute the value of  $I_B$  in equation (1)

$$V_{TH} - V_{BE} + V_D = R_E I_C + (R_{TH} + R_E) \left[ \frac{I_C - (1 + \beta) I_{CO}}{\beta} \right]$$

$$\therefore \beta [V_{TH} - V_{BE} + V_D] = \beta R_E I_C + (R_{TH} + R_E) I_C - (1 + \beta) I_{CO} (R_{TH} + R_E)$$

$$\therefore I_C [ \beta R_E + R_{TH} + R_E ] = \beta [V_{TH} - (V_{BE} - V_D)] + (1 + \beta) I_{CO} \frac{(R_{TH} + R_E)}{(R_{TH} + R_E)}$$


$$\therefore I_C = \frac{\beta [V_{TH} - (V_{BE} - V_D)] + (1 + \beta) I_{CO}}{R_{TH} + (1 + \beta) R_E}$$

Since variation in  $V_{BE}$  with temperature is the same as the variation in  $V_D$  with temperature, hence the quantity  $(V_{BE} - V_D)$  remains constant in equation (3).

So  $I_C$  remains constant ~~inspite~~ (4) inspite of variations in  $V_{BE}$ . Although diode compensation for  $V_{BE}$  variation is not perfect yet it is effective in cancelling most of the operating point drift.

(2) Diode compensation for instability due to  $T_C$  variation \*

Used for Germanium transistors.

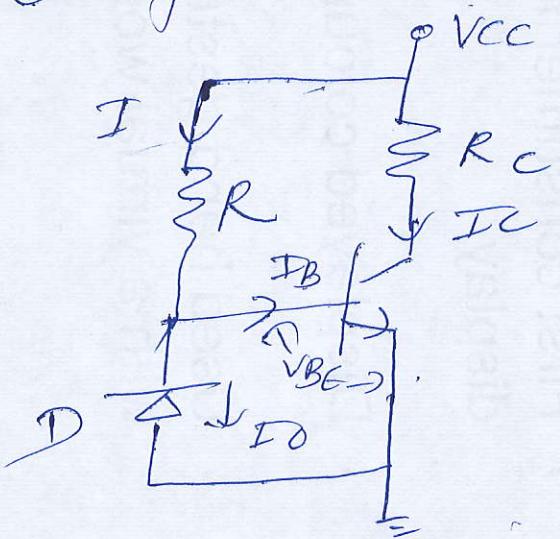

The diode  $D$  and the transistor are of the same type and same material. So the reverse saturation current  $I_D$  of the diode will increase with temperature at the same rate as the transistor collector saturation current  $I_{CO}$ .

$$I = \frac{V_{CC} - V_{BE}}{R} \approx \frac{V_{CC}}{R} = \text{constant} \quad (1)$$

The diode is reverse biased by  $V_{BE}$

$$I_B = I - I_D \quad (2)$$

$$I_C = B I_B + (1+B) I_{CO}$$

In the above equation substitute value of  $I_B$  given by equation ②

$$\therefore I_C = \beta(I - I_D) + (1 + \beta)I_{C0}.$$

$\beta \gg 1$

$$\therefore I_C = BI - BI_D + BI_{C0}$$

$$R = BI - B(I_D - I_{C0}) \quad \dots (3)$$

In expression ③  $I$  is almost constant and if  $I_D$  of diode D and  $I_{C0}$  of transistor trade each other over operating temperature range, then  $I_C$  remains constant.

### (3) Bias compensation using thermistor

(i)


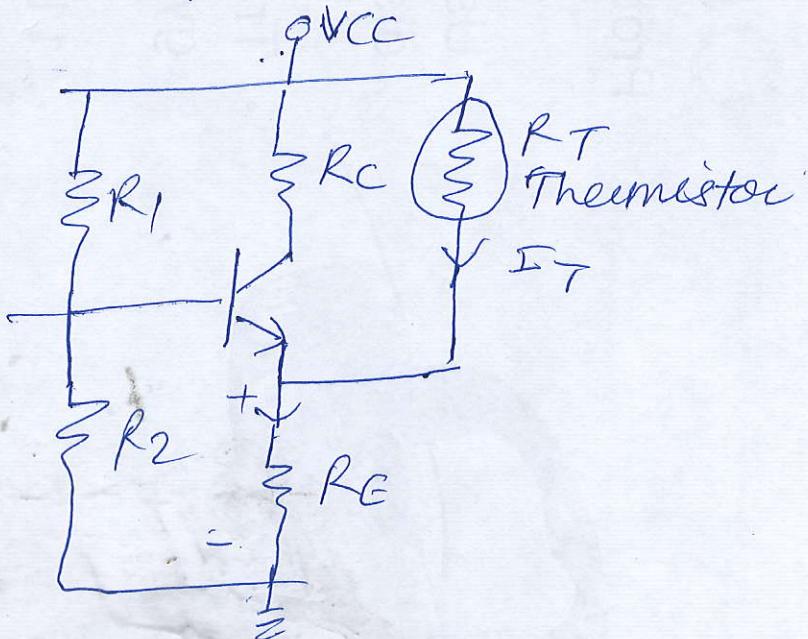


Figure shows the voltage divider bias CE amplifier with thermistor  $R_T$ . The thermistor has a negative temperature coefficient of resistance i.e. its resistance decreases exponentially with increasing

temperature. The thermistor  $R_T$  is used to minimize the increase in  $I_C$  due to changes in  $T_V$ ,  $V_{BE}$  or  $B$  with temperature.

As the temperature increases, resistance  $R_T$  of the thermistor decreases. Therefore current  $I_T$  increases which results in increase in current across  $R_E$ . So the voltage developed across  $R_E$  increases in magnitude. This voltage reverse biases the E junction. As a result  $I_C$  reduces. &  $I_D$  remains fairly constant.

(ii)

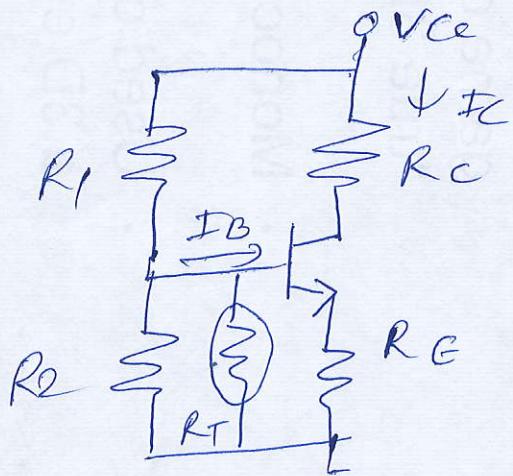

Here thermistor is placed in the B circuit across  $R_2$ . As the temperature increases, the drop across  $R_T$  decreases so the net forward bias of E decreases and consequently  $I_C$  decreases. This reduced  $I_C$  tends to compensate for the increased  $I_C$  caused by the rise in temperature.

#### (4) Transistor compensation

7


Instead of a thermistor, a transistor may be used for operating point stability. Transistor is a temperature sensitive resistor having positive temperature coefficient of resistance.

It is a heavily doped semiconductor.

The transistor may be used in parallel with  $R_1$  or in parallel with ( $C$  or in place of)  $R_E$ .

As the temperature increases the resistance of transistor increases. Thus the resistance of parallel combination ( $R_1 \parallel R_S$ ) increases. Now the voltage drop across  $R_2$  decreases due to decrease of this voltage the net forward emitter bias decreases.

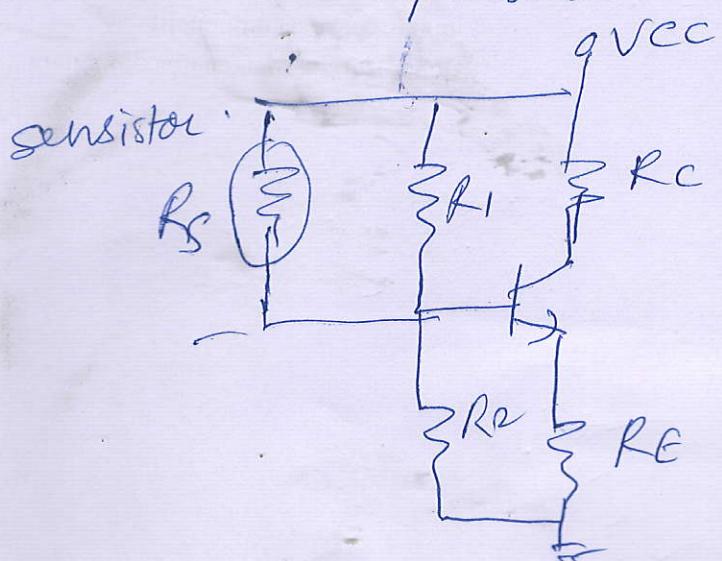As a result  $I_C$  decreases. This reduced  $I_C$  compensates for the increased  $I_C$  caused by the increase in  $T_{Q0}$ ,  $V_{BE}$  &  $\beta$  due to temperature.



## (8)

### THERMAL RESISTANCE

Transistor is a temperature dependent device. In order to keep the temperature within the limits, the heat generated must be dissipated to the surrounding. Most of the heat is produced at the C junction. If the temperature exceeds the permissible limit, this junction is destroyed and the transistor is rendered useless.

Consider a transistor operating in open air. Let  $T_A$  = ambient temp i.e. the temperature of surrounding air around transistor.

$T_j$  = the temperature of C-B junction

As  $T_j > T_A$ , difference  $T_j - T_A$  is greater, the power dissipated in the transistor  $P_D$  will be greater.

$$\therefore T_j - T_A \propto P_D$$

$$T_j - T_A = (\textcircled{H}) P_D \dots \textcircled{1}$$

where  $(\textcircled{H})$  is constant of proportionality and is called as thermal resistance or resistance to heat flow from the junction to surrounding air.

$$(\textcircled{H}) = \frac{T_j - T_A}{P_D}$$

Unit of  $(\textcircled{H})$  is  $^{\circ}\text{C}/\text{Watt}$

(9)

Value of  $\Theta_{\text{J}}$  depends on

- (i) Size of transistor
- (ii) Convection or radiation to the surroundings
- (iii) forced air cooling (if used)
- (iv) thermal connection of the device to a metal chassis or heat sink.

### Thermal runaway:

The maximum power  $P_{D\text{max}}$  which a transistor can dissipate depends on the transistor construction & may lie in the range from few mw to 200 w. Max. power is limited by the temp. that C-B junction can withstand.

For Si Transistors 150 to 225°C & for Ge Transistors 60 to 100°C.

Junction temp. may rise due to ambient temp. rise or self heating which results from the power dissipated at the C-B junction.

As a consequence of junction ~~temp.~~ power dissipation, the junction temp. rises and this in turn increases the  $T_c$  with a subsequent increase in power dissipation. This phenomenon is referred as thermal runaway and if continued it may result in permanently damaging the transistor.

## Condition for thermal stability

For a transistor, it is necessary to avoid thermal runaway. The thermal stability of a transistor is defined as the ability of a transistor to avoid thermal runaway.

Therefore the required condition is that the rate at which heat is produced at the C-B junction must not exceed the rate at which heat can be dissipated

$$\therefore \frac{\partial P_C}{\partial T_J} < \frac{\partial P_D}{\partial T_J} \quad \dots (1)$$

$$T_J - T_A = \textcircled{H} P_D$$

Differentiating above equation w.r.t.  $T_J$

$$1 = \textcircled{H} \frac{\partial P_D}{\partial T_J} \quad \dots$$

$$\frac{\partial P_D}{\partial T_J} = \frac{1}{\textcircled{H}} \quad \dots (2)$$

From equation (1) & (2).

The condition to prevent thermal runaway is

$$\boxed{\frac{\partial P_C}{\partial T_J} < \frac{1}{\textcircled{H}}}$$

$$\frac{\partial P_C}{\partial T_J} \times \frac{\partial I_C}{\partial I_C} < \frac{1}{\textcircled{H}}$$

$$\therefore \frac{\partial P_C}{\partial I_C} \times \frac{\partial I_C}{\partial T_J} < \frac{1}{\textcircled{H}} \quad \dots (3)$$

Consider voltage divider bias, The value of  $P_C$  heat produced is given by. (11)

$$P_C = V_{CC} I_C - I_C^2 R_C - I_E^2 R_E.$$

$$\text{or } P_C = V_{CC} I_C - I_C^2 (R_C + R_E) \quad (\text{TEST})$$

$V_{CC} I_C$  is power taken from supply  $V_{CC}$ .

$$\therefore \frac{\partial P_C}{\partial I_C} = V_{CE} - 2I_C (R_C + R_E). \quad (2)$$

Rewriting equation (3)

$$\frac{\partial P_C}{\partial I_C} < \frac{1}{T_j} \quad (4)$$

In this equation (4),  $\frac{\partial I_C}{\partial T_j}$  are positive, therefore the condition (4) is always satisfied if  $\frac{\partial P_C}{\partial I_C}$  is negative

$$\frac{\partial P_C}{\partial I_C} = V_{CC} - 2I_C (R_C + R_E)$$

$$\therefore V_{CC} < 2I_C (R_C + R_E) \quad (5)$$

$$\therefore \frac{V_{CC}}{2} < I_C (R_C + R_E)$$

$$\therefore I_C > \frac{V_{CC} \cancel{(R_C + R_E)}}{2(R_C + R_E)}$$

$$\text{As } V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$\therefore I_C (R_C + R_E) = V_{CC} - V_{CE}. \quad (6)$$

Substituting value of  $I_C (R_C + R_E)$  in equation 5

$$\frac{V_{CC}}{2} < V_{CC} - V_{CE}$$

(12)

$$\therefore V_{CG} < V_{CC} - \frac{V_{CE}}{2}$$

$$V_{CE} < \frac{V_{CC}}{2} \quad (7)$$

Thus if  $V_{CE} < \frac{V_{CC}}{2}$  stability is ensured