
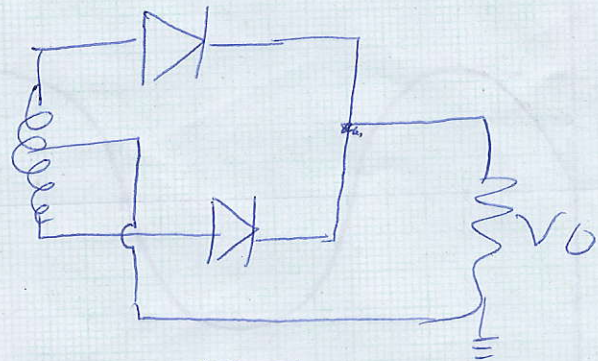



## (2) FULL WAVE RECTIFIER

A full wave rectifier is a circuit which allows a unidirectional current to flow through the load during the entire input cycle.

## (a) CENTRE-TAPPED FULL WAVE RECTIFIER

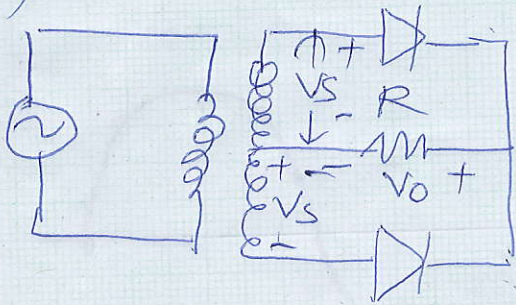

[OR]

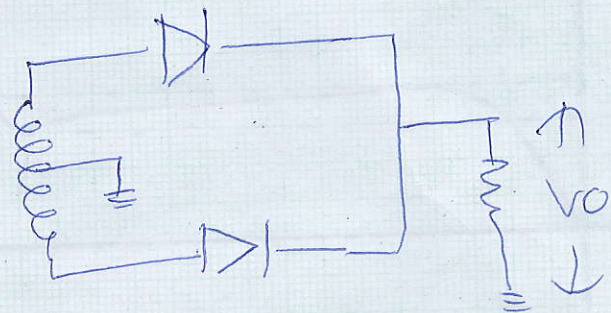


Construction: The circuit uses 2 diodes which are connected to the centre-tapped secondary winding of the transformer. The input signal is applied to the primary winding of the transformer. The center tap is taken as the ground or zero voltage reference point. The voltage between the center tap and either ~~to~~ end of the secondary winding is half of the secondary voltage.  $V_s = \frac{V_2}{2}$



2


Working:

(i) +ve half cycle:  $D_1$

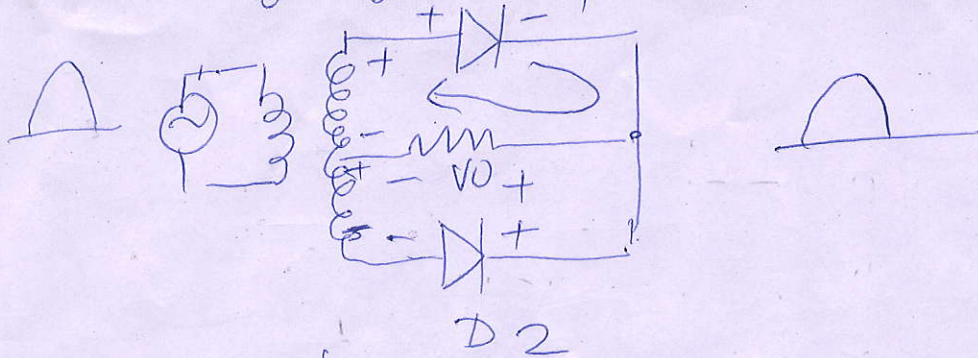


Diode  $D_1$  is forward biased and diode  $D_2$  is reverse biased. As a result  $D_1$  conducts and  $D_2$  is OFF.  $D_1$  supplies the load current.

(ii) -ve half cycle:

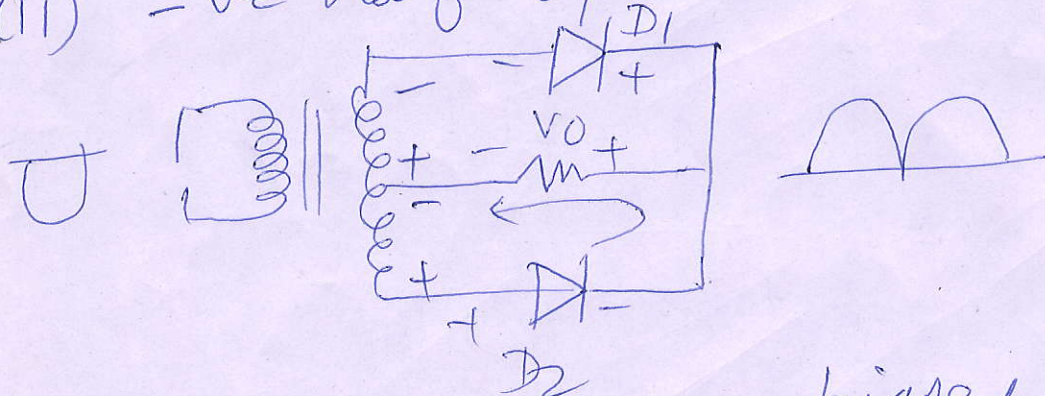

Diode  $D_1$  is reverse biased and  $D_2$  is forward biased.  $D_1$  is OFF and  $D_2$  conducts.  $D_2$  supplies load current.

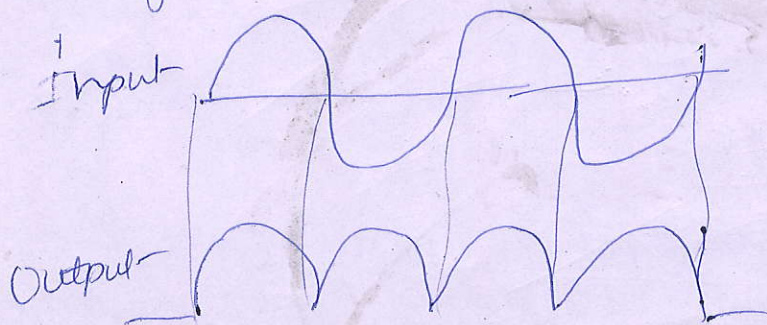During both cycles the current flowing through the load is in same direction.





## PARAMETERS

3

- (1) AVERAGE OR D.C. VALUE OF O/P VOLTAGE  
 $V_{dc} = \frac{\text{Area under the curve over half cycle}}{\pi}$

$$\begin{aligned} &= \frac{\int_0^\pi v \, d\theta}{\pi} = \frac{\int_0^\pi \text{Base } V_m \sin \theta \, d\theta}{\pi} \\ &= \frac{V_m}{\pi} (-\cos \theta)_0^\pi = \frac{V_m}{\pi} (+1 - (-1)) \\ &= \frac{2V_m}{\pi} = 0.636 V_m \end{aligned}$$

- (2) Average or d.c. value of load current

$$I_{dc} = \frac{V_{dc}}{R_L} = \frac{2V_m}{\pi R_L} = \frac{2I_m}{\pi} = 0.636 V_m$$

- (3) RMS VALUE OF LOAD CURRENT.

$$\begin{aligned} I_{rms} &= \sqrt{\frac{2}{2\pi} \int_0^\pi i^2 \, d\theta} \\ &= \sqrt{\frac{1}{\pi} \int_0^\pi I_m^2 \sin^2 \theta \, d\theta} \\ &= \sqrt{\frac{I_m^2}{\pi} \int_0^\pi \left( \frac{1 - \cos 2\theta}{2} \right) d\theta} \\ &= \sqrt{\frac{I_m^2}{2\pi} \left[ \int_0^\pi d\theta - \int_0^\pi \cos 2\theta \, d\theta \right]} \\ &= \sqrt{\frac{I_m^2}{2\pi} \left[ \theta \right]_0^\pi - \left[ \frac{\sin 2\theta}{2} \right]_0^\pi} \\ &= \sqrt{\frac{I_m^2}{2\pi} \times \pi} = \sqrt{\frac{I_m^2}{2}} = \frac{I_m}{\sqrt{2}} \end{aligned}$$



(4)

(4) RIPPLE FACTOR

$$I_{dc} = \frac{2 I_m}{\pi}, \quad I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{I_m}{\sqrt{2}}\right)^2 \times \left(\frac{\pi}{2 I_m}\right)^2 - 1}$$

$$= \sqrt{\frac{I_m^2}{2} \times \frac{\pi^2}{4 I_m^2} - 1} = \sqrt{\frac{\pi^2}{8} - 1}$$

$$= 0.482$$

(5) RATIO OF RECTIFICATION

$$\eta = \frac{I_{dc}^2 R_L}{I_{rms}^2 (R_f + R_L)}$$

$$= \frac{\left(\frac{2 I_m}{\pi}\right)^2 \times R_L}{\left(\frac{I_m}{\sqrt{2}}\right)^2 (R_f + R_L)}$$

$$= \frac{4 I_m^2}{\pi^2} \times \frac{R_L \times 2}{I_m^2 (R_f + R_L)}$$

$$= \frac{8}{\pi^2} \frac{R_L}{R_f + R_L} = \frac{0.812}{1 + \frac{R_f}{R_L}}$$

$$R_L \gg R_f$$

$$\therefore \eta = 0.812$$



(6) Peak Inverse voltage rating of diode (5)  
Voltage across reverse biased diode  
= voltage across half the secondary  
+ voltage across  $R_L$   
=  $V_m + V_m = 2V_m$ .  
 $\therefore$  P.I.V. of diode =  $2V_m$ .

(7) Form Factor

$$F = \frac{I_{rms}}{I_{dc}} = \frac{I_m/\sqrt{2}}{2I_m/\pi} = \frac{\pi}{2\sqrt{2}}$$

$$F = 1.11$$

Advantages

- (1) The d.c. output voltage and load current values are twice than those of a half wave rectifier.
- (2) The ripple factor is much less than (0.482) that of a Half wave rectifier (1.21)
- (3) The efficiency is twice that of a Half wave rectifier.




Disadvantages:

- (1) The output voltage is half of the sec. voltage.
- (2) The P.I.V. rating of a diode is twice that of the diode used in half wave rectifier.
- (3) Expensive to manufacture a centre-tapped



transformer which produces equal voltages on each half of the secondary winding

## (b) FULL WAVE BRIDGE RECTIFIER

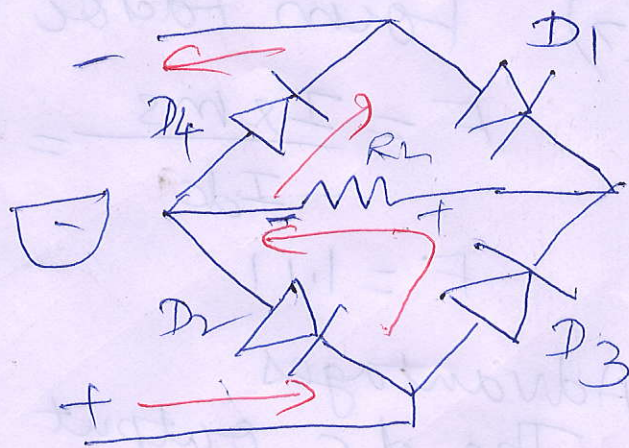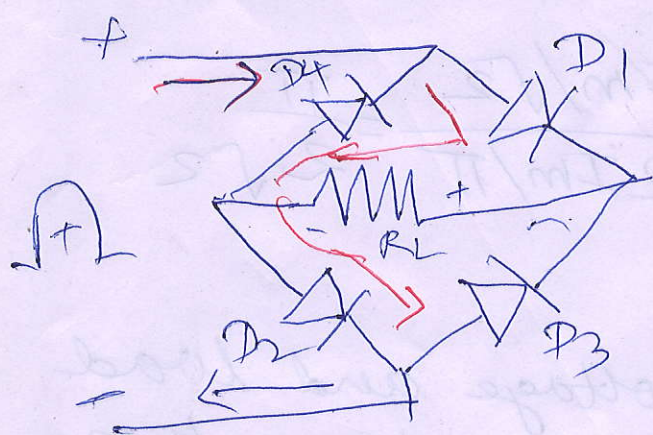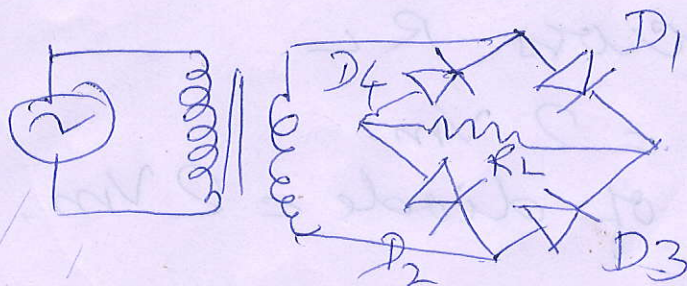

Working:

(i) +ve half cycle.

Diodes  $D_1$  &  $D_2$  are forward biased and conduct some current due to which a voltage is developed across  $R_L$ .  $D_3$  and  $D_4$  are reverse biased.

(ii) -ve half cycle:

Diodes  $D_3$  and  $D_4$  are forward biased & conduct current in the same direction through  $R_L$  as during +ve half cycle,  $D_1$  &  $D_2$  are reverse biased.


As a result a full rectified output voltage is developed across  $R_L$ .



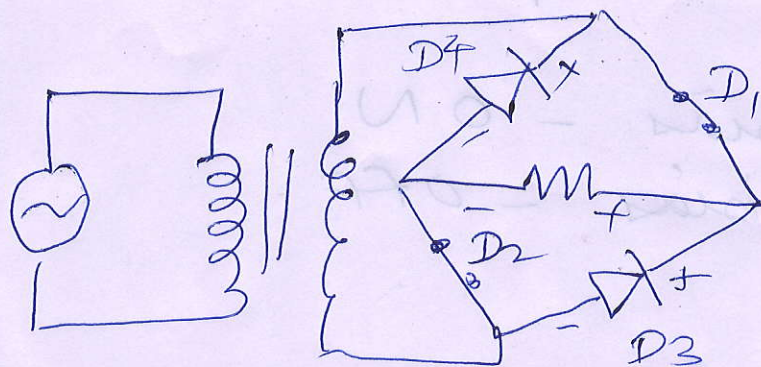(7)

All the parameters of Bridge rectifier are same as full wave center-tapped rectifier

P.I.V rating of diode in Bridge rectifier



Here  $D_1$  &  $D_2$  are forward biased, whereas  $D_3$  &  $D_4$  are reverse biased and have maximum reverse bias voltage equal to the maximum secondary voltage

$V_m$  + voltage across  $R_L$  ( $\text{max } V_m$ )

$\therefore$  Across each diode  $D_4$  &  $D_3$

The voltage is  $= \frac{2V_m}{2} = V_m$ .

$\therefore$  The P.I.V. rating of diode  $= V_m$ .

Advantages of Bridge rectifier

1. The transformer is less costly as it is required to provide only half the voltage of an equivalent center tapped rectifier.



2. No center tap is required on transformer  
3. P.I.V. rating of diode is less.

### Disadvantages

1. Uses 4 diodes

Diode has an important application as a switch.

- (1) Forward bias - ON  
(2) Reverse bias - OFF